

# EV2005DD-00B

500mA Low-Current LDO Linear Regulator EV Board

#### DESCRIPTION

The EV2005DD-00B evaluation board demonstrates the performance of MP2005, a monolithic low-current, low-dropout LDO linear regulator. It operates from a 2.5V to 5V input bias voltage and regulates the output voltage from as low as 0.5V.

The EVB can supply up to 500mA of load current with a typical dropout voltage of 75mV. It requires a bias supply (2.5V to 5.5V) separate from  $V_{\text{IN}}$  to run the internal reference and LDO drive circuitry. The output current comes directly from the input voltage supply for high efficiency regulation. The 0.5V internal reference voltage allows the output to be programmed to a range of 0.5V to 5V.

The EV2005DD-00B provides thermal overload and current limit protection, stability with ultra low ESR ceramic capacitors as low as 1uF, and fast transient response. The MP2005 is available in a 8-pin QFN (2mm x 3mm) package and is also available in fixed output voltage versions.

#### **ELECTRICAL SPECIFICATIONS**

Parameter	Symbol	Value	Units
Input Voltage	$V_{IN}$	1.0 – 5	V
Blas Voltage	VB	5	V
Output Current	I <sub>OUT</sub>	0.5	Α
Output Voltage	$V_{OUT}$	1.8	V

### **FEATURES**

- Wide 1.0V to 5V Input Voltage Range
- Stable with Very Small Ceramic Capacitors
- 75mV Dropout at 500mA Output
- 2% Accurate Output Voltage
- Adjustable Output Range from 0.5V to 5V
- Low Noise: 80µV<sub>RMS</sub> (10Hz to 100KHz)
- High PSRR: 40dB at 1MHz
- Stable With Low-ESR Output Capacitors
- Low 100µA Ground Current
- Internal Thermal Protection
- Current Limit Protection
- Fully Assembled and Tested

#### **APPLICATIONS**

- Low Current Regulators
- Low Power Handheld Devices
- Battery Powered Systems
- Cellular Phones
- Portable Electronic Equipment
- Post Regulation for Switching Power Supplies
- Power Supplies


"MPS" and "The Future of Analog IC Technology", are Registered Trademarks of Monolithic Power Systems, Inc.

#### **EV2005DD-00B EVALUATION BOARD**




L x W x H) 2.9" x 2.9" x 0.5" (7.5cm x 7.5cm x 1.2cm)

Board Number	MPS IC Number		
EV2005DD-00B	MP2005		

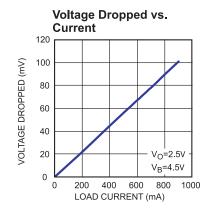



## **EVALUATION BOARD SCHEMATIC**

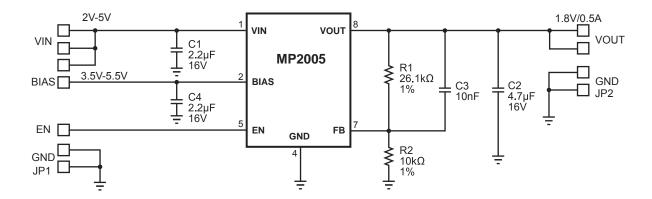

## **EV2005DD-00B BILL OF MATERIALS**

Qty	Ref	Value	Description	Package	Manufacturer	Manufacturer P/N
2	C1, C4	2.2µF	Ceramic Cap., X7R, 16V	1206	TDK	C3216X7R1C225K
1	C2	4.7µF	Ceramic Cap., X7R, 16V	1206	TDK	C3216X7R1C475K
1	С3	10nF	Ceramic Cap X7R, 50V	603	TDK	GRM188R71H103KA
1	R1	26.1kΩ	Film Res., 1%	603	Panasonic	ERJ-3EKF2612V
1	R2	10kΩ	Film Res., 1%	603	Panasonic	ERJ-3EKF1002V
1	JP		10-Pin Header, 0.1"		Sullins	PTC08SAAN
1	JP		5-Pin Header, 0.1"		Sullins	PTC08SAAN
1	U1		Linear Regulator	QFN-8	MPS	MP2005DD



## PRINTED CIRCUIT BOARD LAYOUT

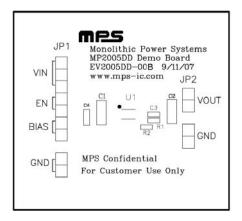


Figure 1—Top Silk Layer

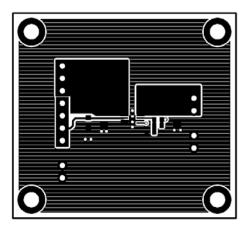


Figure 2—Top Layer

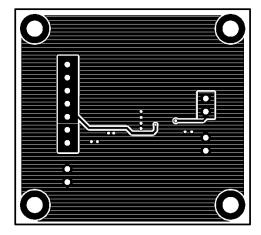


Figure 3—Bottom Layer



## **QUICK START GUIDE**

The output voltage of this board is set to 1.8V. The EN pin is connected to BIAS with a jumper for automatic startup. You can connect EN to GND to disable the MP2005

- 1. Attach the positive and negative ends of the load to the VOUT and GND pins, respectively.
- 2. Attach the input voltage (2V  $\leq$  V<sub>IN</sub>  $\leq$  5V) and input ground to the VIN and GND pins, respectively.
- 3. Attach the BIAS voltage (3.5V  $\leq$  V<sub>BIAS</sub>  $\leq$  5.5V) and BIAS ground to the BIAS and GND pins, respectively.
- 4. The VIN voltage and BIAS voltage can be set up to same voltage but it has to meet:

$$V_{IN}=V_{BIAS}>(1.8V + V_{OUT})$$
 and  $V_{BIAS}>2.7V$ 

5. The default resistor values on the board are R1=26.1k $\Omega$  and R2=10k $\Omega$ . Changing these resistor values will change the output voltage. Use the following equation to determine resistor values for different output voltages:

$$V_{OUT} = 0.5Vx(1 + \frac{R1}{R2})$$

**NOTICE:** The information in this document is subject to change without notice. Users should warrant and guarantee that third party Intellectual Property rights are not infringed upon when integrating MPS products into any application. MPS will not assume any legal responsibility for any said applications.